

CHAITANYA BHARATHI INSTITUTE OF TECHNOLOGY (Autonomous)
BE (CSE & & IT) II/IV I Sem (Suppl) Examination May – Jun 2016

Basic Electronics

Time: 3 Hours

Max Marks:75

Note: Answer all questions from **Section-A** at one place in the same order
 Answer any **five** questions from **Section-B**

Section - A (25 Marks)

- 1 Draw the V-I Characteristics of P-N Junction diode (2)
- 2 Define PIV of P-N junction diode (2)
- 3 List out the Zener Diode characteristics (2)
- 4 Draw the h-parameter equivalent circuits for CE amplifier and label it (3)
- 5 List out the properties of negative feedback amplifiers (2)
- 6 Draw the RC Type- Phase shift oscillator and also write formula for the frequency of oscillations (3)
- 7 Write the Practical characteristics of an OPAMP (3)
- 8 Draw the basic gates with Universal gates (3)
- 9 Draw the circuit and the characteristics of SCR (2)
- 10 Differentiate between LED and LCD (3)

Section - B (50 Marks)

- 11 (a) Discuss the electric properties of Ge and Si (5)
 - (b) Draw and explain operation of the full wave Bridge rectifier (5)
 - 12 (a) Derive the expressions for A_i, A_v, R_i, R_o of the CE Amplifier (7)
 - (b) Explain the Zener break down mechanism (3)
 - 13 (a) Explain the transfer characteristics of JFET (5)
 - (b) Explain the effect of negative feedback on Input impedance and Output impedance (5)
 - 14 (a) With neat block diagram, explain the RC-phase shift oscillator. (5)
 - (b) Define the term Voltage regulation and explain the application as voltage regulator (5)
 - 15 (a) Draw the circuit diagram of OPAMP integrator and Differentiator. Also derive the expressions for output? (10)
 - 16 (a) State and prove Demorgan's Theorem (5)
 - (b) Simplify and draw the logic diagram for the given expression (5)
- $$F = \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABC} + \overline{ABC}.$$
- 17 (a) Explain about the classification of transducers (5)
 - (b) Explain about UJT Relaxation Oscillator (5)
